

## EXPERIMENT 5

### MOORE AND MEALY MACHINES


**AIM OF THE EXPERIMENT:** To determine residues of a positive binary number modulo 5 using mealy and moore machines.

**TRUTH TABLE, CIRCUIT DIAGRAM and STATE DIAGRAM:**

#### MEALY MACHINE

**Part A: Number given serially from MSB**

#### STATE DIAGRAM

 

#### Mealy Machine with start state 0

As the input  $x$  is received the machine makes corresponding transitions and outputs the corresponding values.

Formally

$$M = (Q, \Sigma, \Delta, S_0, \delta, \lambda)$$

$$Q = \{S_0, S_1, S_2, S_3, S_4\}$$

$$\Sigma = \{0, 1\}$$

$$\Delta = \{0, 1, 2, 3, 4, 5\}$$

$$\delta(q, a) = (2q + a) \bmod 5$$

$$\lambda(q, a) = q$$

### Excitation table


$y_2$	$y_1$	$y_0$	$x$	$Y_2$	$Y_1$	$Y_0$	$z_2$	$z_1$	$z_0$
0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0	0	1
0	0	1	0	0	1	0	0	1	0
0	0	1	1	0	1	1	0	1	1
0	1	0	0	1	0	0	1	0	0
0	1	0	1	0	0	0	0	0	0
0	1	1	0	0	0	1	0	0	1
0	1	1	1	0	1	0	0	1	0
1	0	0	0	0	1	1	0	1	1
1	0	0	1	1	0	0	1	0	0

$$Y_0 = y_2' y_1 x' + y_2 x + y_1 y_0 x'$$

$$Y_1 = y_2 x' + y_2 x + y_1' y_0$$

$$Y_2 = y_2 x + y_1 y_0' x'$$

$$z_i = y_i$$

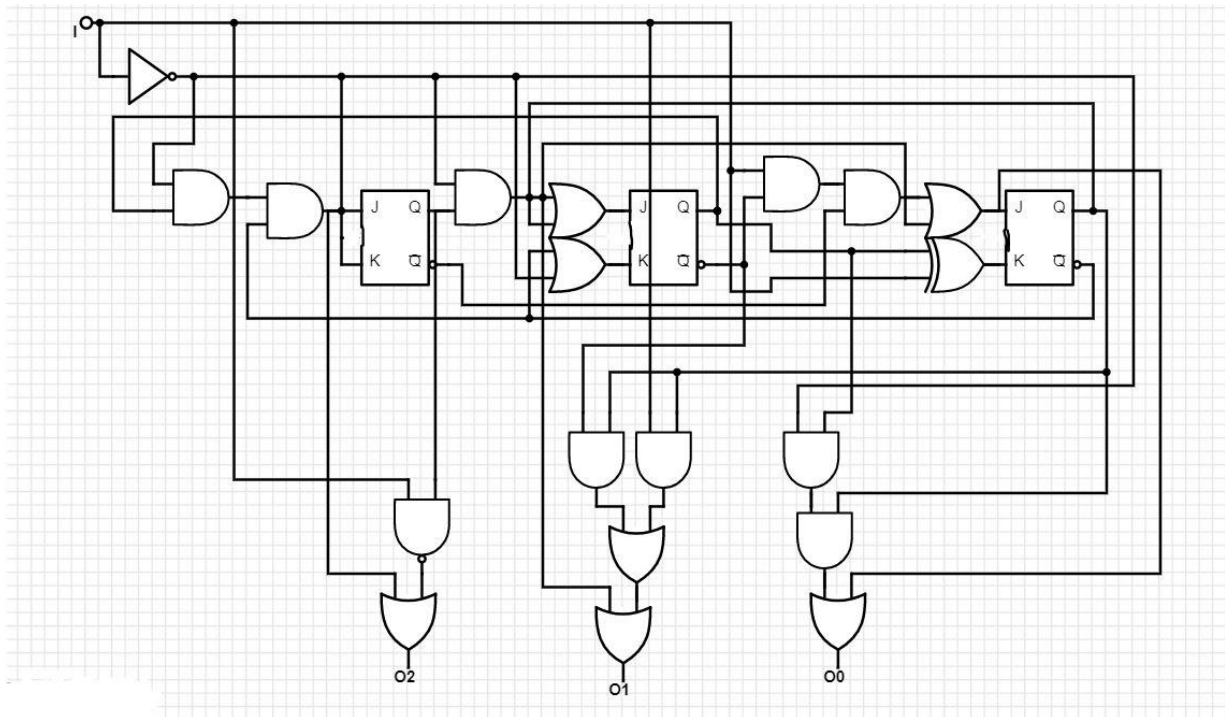

## Verilog code

```
module msb_mealy (x, clk, reset, z);
    input x, clk, reset;
    output reg [2:0] z;
    parameter S0=0, S1=1, S2=2, S3=3, S4=4;
    reg [2:0] PS;
    always @(posedge clk or posedge reset)
        if (reset)
            PS <= S0;
        else
            case (PS)
                S0: begin
                    z = x ? 3'b001 : 3'b000;
                    PS <= x ? S1 : S0;
                end
                S1: begin
                    z = x ? 3'b011 : 3'b010;
                    PS <= x ? S3 : S2;
                end
                S2: begin
                    z = x ? 3'b000 : 3'b100;
                    PS <= x ? S0 : S4;
                end
                S3: begin
                    z = x ? 3'b010 : 3'b001;
                    PS <= x ? S2 : S1;
                end
                S4: begin
                    z = x ? 3'b100 : 3'b011;
                    PS <= x ? S4 : S3;
                end
            endcase
    endmodule
```

```
module msb_mealy_test;
    reg clk, x, reset;
    wire [2:0] z;
    msb_mealy mm (x, clk, reset, z);
    initial
        begin
            $dumpfile("msb_mealy.vcd");
            $dumpvars(0,msb_mealy_test);
            clk=1'b0; reset=1'b1;
            #15 reset=1'b0;
        end
    always #5 clk= ~clk;
    initial
```

```

begin
    #12 x=1; #10 x=0; #10 x=1; #10 x=0; #10 x=1;
    #10 x=0; #10 x=0; #10 x=1; #10 x=0; #10 x=1;
    #10 $finish;
end
endmodule


```

### Part B: Number given serially from LSB

Logic: Say the residue upto current read number is  $r$  and no. of digits read is  $l$ . Then the next output would be  $= (2^l * b_l + r) \bmod 5$

Now,  $2^l \bmod 5$  cycles between 4 values 1,2,4 and 3 in this order. So, we maintain 20 states + 1 start state for this mealy machine.

### STATE DIAGRAM

 

Formally

$$M = (Q, \Sigma, \Delta, S_{00}, \delta, \lambda)$$

$$Q = \{S_{00}, S_{01}, \dots, S_{03}, \dots, S_{43}\}$$

$$\Sigma = \{0, 1\}$$

$$\Delta = \{0, 1, 2, 3, 4\}$$

$$\delta(q, a) = (q(\text{left digit}) + 2^{q(\text{right digit})} * b) \bmod 5$$

$$\Delta(q, a) = q(\text{left digit})$$

Verilog code:

```

module lsb_mealy (x, clk, reset, z);
    input x, clk, reset;
    output reg [2:0] z;
    parameter start=0;
    parameter zero1=1, zero2=2, zero4=3, zero3=4;
    parameter one1=5, one2=6, one4=7, one3=8;
    parameter two1=9, two2=10, two4=11, two3=12;
    parameter three1=13, three2=14, three4=15, three3=16;
    parameter four1=17, four2=18, four4=19, four3=20;
    reg [4:0] state;
    always @(posedge clk or posedge reset)
        if (reset)
            state <= start;
        else
            case (state)
                start: begin
                    state <= x ? one1 : zero1;
                    z = x ? 1 : 0;
                end
                zero1: begin
                    state <= x ? two2 : zero2;
                    z = x ? 2 : 0;
                end
                zero2: begin
                    state <= x ? four4 : zero4;
                    z = x ? 4 : 2;
                end
                zero4: begin
                    state <= x ? three3 : zero3;
                    z = x ? 3 : 0;
                end
                zero3: begin
                    state <= x ? one1 : zero1;
                    z = x ? 1 : 0;
                end
                one1: begin
                    state <= x ? three2 : one2;
                    z = x ? 3 : 1;
                end
                one2: begin
                    state <= x ? zero4 : one4;
                    z = x ? 0 : 1;
                end
                one4: begin
                    state <= x ? four3 : one3;

```

```

                                z= x ? 4 : 1;
                                end
one3: begin
                                state <= x ? two1 : one1;
                                z= x ? 2 : 1;
                                end

two1: begin
                                state <= x ? four2 : two2;
                                z= x ? 4 : 2;
                                end
two2: begin
                                state <= x ? one4 : two4;
                                z= x ? 1 : 2;
                                end
two4: begin
                                state <= x ? zero3 : two3;
                                z= x ? 0 : 2;
                                end
two3: begin
                                state <= x ? three1 : two1;
                                z= x ? 3 : 2;
                                end

three1: begin
                                state <= x ? zero2 : three2;
                                z= x ? 1 : 3;
                                end
three2: begin
                                state <= x ? two4 : three4;
                                z= x ? 2 : 3;
                                end
three4: begin
                                state <= x ? one3 : three3;
                                z= x ? 1 : 3;
                                end
three3: begin
                                state <= x ? four1 : three1;
                                z= x ? 4 : 3;
                                end

four1: begin
                                state <= x ? one2 : four2;
                                z= x ? 1 : 4;
                                end
four2: begin
                                state <= x ? three4 : four4;
                                z= x ? 3 : 4;

```

```

                                end
                                four4: begin
                                    state <= x ? two3 : four3;
                                    z = x ? 2 : 4;
                                end
                                four3: begin
                                    state <= x ? zero1 : four1;
                                    z = x ? 0 : 4;
                                end
                                end
                                endcase
endmodule

```

```


module lsb_mealy_test;
    reg clk, x, reset;
    wire [2:0] z;
    lsb_mealy lm (x, clk, reset, z);
    initial
        begin
            $dumpfile("lsb_mealy.vcd");
            $dumpvars(0, lsb_mealy_test);
            clk = 1'b0; reset = 1'b1;
            #15 reset = 1'b0;
        end
    always #5 clk = ~clk;
    initial
        begin
            #12 x = 1; #10 x = 0; #10 x = 1; #10 x = 0; #10 x = 0;
            #10 x = 1; #10 x = 0; #10 x = 1; #10 x = 0; #10 x = 1;
            #10 $finish;
        end
endmodule

```

## MOORE MACHINE

### Part A: Number serially from MSB

#### STATE DIAGRAM

 

The logic is same as that of the Mealy machine, except that the output is corresponding to the state the machine is in.

#### Verilog code

```
module msb_moore (x, clk, reset, z);

    input x, clk, reset;
    output reg [2:0] z;
    parameter S0=0, S1=1, S2=2, S3=3, S4=4;
    reg [2:0] state;
    always @(posedge clk or posedge reset)
        if (reset)
            state <= S0;
        else
            case (state)
                S0: state <= x ? S1 : S0;
                S1: state <= x ? S3 : S2;
                S2: state <= x ? S0 : S4;
                S3: state <= x ? S2 : S1;
                S4: state <= x ? S4 : S3;
            endcase
    always @(state)
        case (state)
            S0: z=3'b000;
            S1: z=3'b001;
            S2: z=3'b010;
            S3: z=3'b011;
            S4: z=3'b100;
        endcase
endmodule
```




```

module msb_moore_test;
    reg clk, x, reset;
    wire [2:0] z;
    msb_moore mm (x, clk, reset, z);
    initial
        begin
            $dumpfile("msb_moore.vcd");
            $dumpvars(0,msb_moore_test);
            clk=1'b0; reset=1'b1;
            #15 reset=1'b0;
        end
    always #5 clk= ~clk;
    initial
        begin
            #12 x=1; #10 x=0; #10 x=1; #10 x=0; #10 x=1;
            #10 x=0; #10 x=0; #10 x=1; #10 x=0; #10 x=1;
            #10 $finish;
        end
    end
endmodule

```

## Part B: Number serially from LSB

### STATE DIAGRAM

 

The state machine is the same as the mealy machine, except that the output corresponding to each state is fixed.

### Verilog code:

```
module lsb_moore (x, clk, reset, z);
    input x, clk, reset;
    output reg [2:0] z;
    parameter start=0;
    parameter zero1=1, zero2=2, zero4=3, zero3=4;
    parameter one1=5, one2=6, one4=7, one3=8;
    parameter two1=9, two2=10, two4=11, two3=12;
    parameter three1=13, three2=14, three4=15, three3=16;
    parameter four1=17, four2=18, four4=19, four3=20;
    reg [4:0] state;
    always @(posedge clk or posedge reset)
        if (reset)
            state <= start;
        else
            case (state)
                start: state <= x ? one1 : zero1;
                zero1: state <= x ? two2 : zero2;
                zero2: state <= x ? four4 : zero4;
                zero4: state <= x ? three3 : zero3;
                zero3: state <= x ? one1 : zero1;

                one1: state <= x ? three2 : one2;
                one2: state <= x ? zero4 : one4;
                one4: state <= x ? four3 : one3;
                one3: state <= x ? two1 : one1;

                two1: state <= x ? four2 : two2;
                two2: state <= x ? one4 : two4;
                two4: state <= x ? zero3 : two3;
                two3: state <= x ? three1 : two1;

                three1: state <= x ? zero2 : three2;
                three2: state <= x ? two4 : three4;
                three4: state <= x ? one3 : three3;
                three3: state <= x ? four1 : three1;

                four1: state <= x ? one2 : four2;
                four2: state <= x ? three4 : four4;
                four4: state <= x ? two3 : four3;
                four3: state <= x ? zero1 : four1;
            endcase
        always @(state)
            case(state)
                start: z=3'b000;
                zero1: z=3'b000;
                zero2: z=3'b000;
```

```

        zero4: z=3'b000;
        zero3: z=3'b000;

        one1: z=3'b001;
        one2: z=3'b001;
        one4: z=3'b001;
        one3: z=3'b001;

        two1: z=3'b010;
        two2: z=3'b010;
        two4: z=3'b010;
        two3: z=3'b010;

        three1: z=3'b011;
        three2: z=3'b011;
        three4: z=3'b011;
        three3: z=3'b011;

        four1: z=3'b100;
        four2: z=3'b100;
        four4: z=3'b100;
        four3: z=3'b100;
    endcase
endmodule

module lsb_moore_test;
    reg clk, x, reset;
    wire [2:0] z;
    lsb_moore lm (x, clk, reset, z);
    initial
        begin
            $dumpfile("lsb_moore.vcd");
            $dumpvars(0,lsb_moore_test);
            clk=1'b0; reset=1'b1;
            #15 reset=1'b0;
        end
    always #5 clk= ~clk;
    initial
        begin
            #12 x=1; #10 x=0; #10 x=1; #10 x=0; #10 x=0;
            #10 x=1; #10 x=0; #10 x=1; #10 x=0; #10 x=1;
            #10 $finish;
        end
endmodule

```

## RESULTS

The same input in binary is given in all 4 test cases, i.e.  $(1010100101)_2$  and the corresponding remainders at each stage of corresponding mealy and moore machines are consistent.

## DISCUSSION

- To implement each machine, we have mentioned a procedural code. It automatically creates memory elements (D-flip-flops) for each state and each output.
- We can visualize each state for MSB machine as  $y_2y_1y_0$  binary number and we can consider their excitation tables too for their corresponding state transitions consistent with input and their previous values.
- We have intentionally given in input after 2 secs of the positive edge of the clock, so that there is no ambiguity in case of the machine to recognize the input or the state.
- The output is obtained on implementing the Verilog code in gtk wave.

Prepared by-Group2  
Somnath Jena  
Soumitra Das